



B. E.(with Credits)-Regular-Semester 2012-Electronics Engineering Sem. - IV  
**EN 402 Digital Circuits & Fundamentals of Microprocessor**

P. Pages : 2

Time : Three Hours

Max. Marks : 80

Notes :

1. All questions carry as indicated marks.
2. Assume suitable data wherever necessary.
3. Illustrate your answers wherever necessary with the help of neat sketches.

1. a) Simplify the following using k-map. **8**
- i)  $f(A, B, C, D, E) = \sum m(0, 3, 4, 6, 8, 20, 21) + d(7, 9, 10, 25, 27, 31)$
- ii)  $f(A, B, C, D) = A\bar{B}CD + \bar{A}BC + ACD + \bar{B}\bar{C}\bar{D} + \bar{C}D$
- b) Design a BCD to excess-3 code converter. Assume 4-bit input arrive at its input terminal. **8**

**OR**

2. a) Design a combinational circuit that will accept 4-bits at binary and generate an output y.  $Y = 1$  when inputs are even number and  $Y = 0$  for otherwise. **8**
- b) Draw the block diagram of full-adder with the help of truth table obtain the logic equations for each output of the full adder. Draw the logic diagram with the help of logic equations. **8**
3. a) Design a combinational circuit for 2-bit magnitude comparator. **8**
- b) With the help of suitable Multiplexer implement the following function  $f(A, B, C, D) = \sum m(0, 1, 3, 6, 8, 9, 11, 13)$  consider D as a input line and A, B and C as a selection lines to the MUX. **8**

**OR**

